

Problem 2 (11)

Consider the following circuit:

